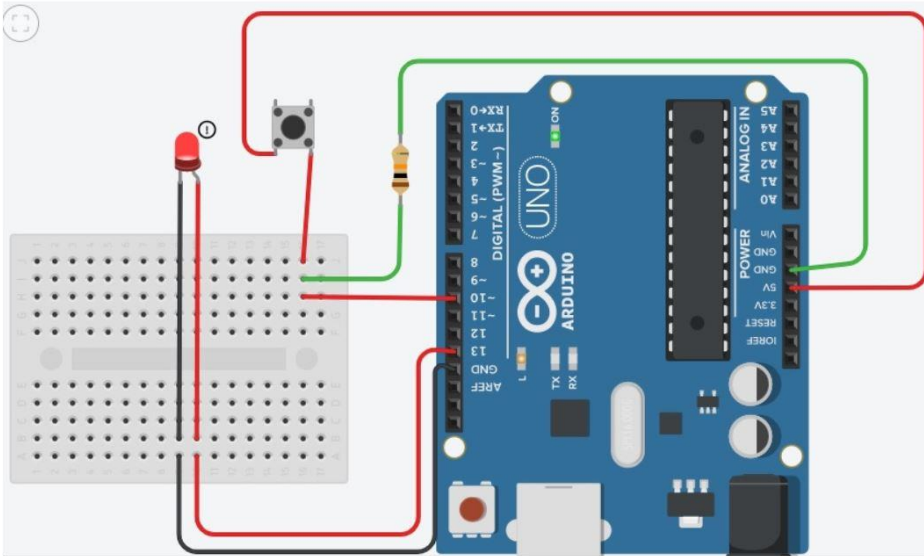


Exp 3

Circuit diagram:



Theory:

Concept used:

Various concepts are used in this experiment as listed:

1. Programming in arduino
2. Connection with switch
3. Working of led with the help of switch.
4. Faradey's law of electromagnetic induction.

Learning and Observations:

In this experiment we learnt about:

1. We learnt about Switch.
2. We learnt about the new command i.e. digitalRead in programing the Arduino Uno.
3. How to blink of LED with the help of switch.

Observations:

1. We observe when we press the switch the start blinking.
2. If we change the delay time in code the blinking time of LED also changes.
3. If we don't connect the ground with the switch, there some current flow even if the switch is not pressed.

4. We can change the pattern of blinking of LED with some changes in code and we can set different patterns with the help of switch.

Precautions:

1. The connections should be proper.
2. The resistance of the ground should be heavier than the resistance of the Arduino Uno board.
3. Some sufficient source of the supply should be connected to the switch.
4. LED should be connected in proper orientation.

Learning Outcomes:

From this experiment we learn and acquire skills about:

1. Algorithms with which we blink LED with the help of switch.
2. A new command `digitalRead`.
3. Importance of ground in branch of switch.